

# 《电路与模拟电子技术》 期末试题 试卷(A)

(考试形式： 闭卷 考试时间：2 小时)



《中山大学授予学士学位工作细则》第六条

考试作弊不授予学士学位

方向：\_\_\_\_\_ 姓名：\_\_\_\_\_ 学号：\_\_\_\_\_

注意：答案一定要写在答卷中，写在本试题卷中不给分。本试卷要和答卷一起交回。

1. (10 pt) For the circuit of Figure 1, compute current  $I_1$ ,  $I_2$ , and  $V_{CD}$ .

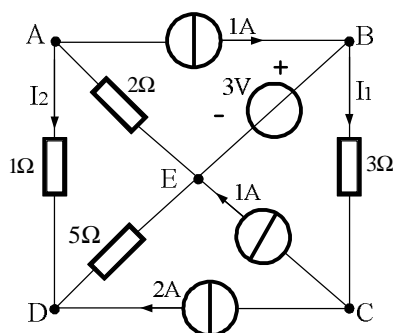


Figure 1

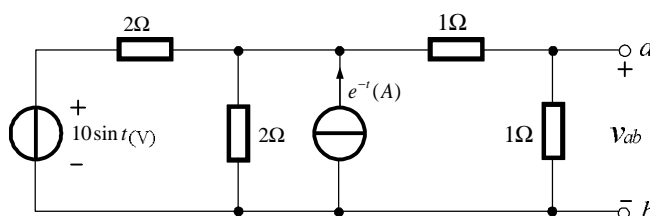


Figure 2

2. (10 pt) Use the superposition theorem to find  $v_{ab}$  in the circuit shown in Figure 2.
3. (15pt) Find the Thevenin equivalent of the network in Figure 3 viewed from  $v$ .

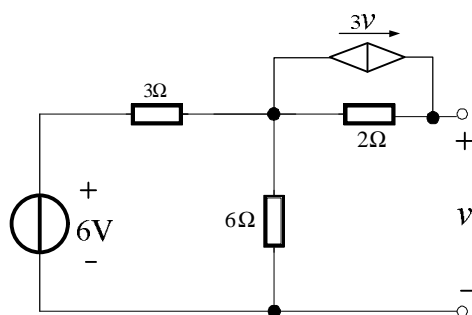


Figure 3

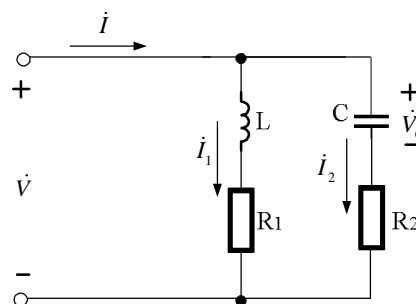


Figure 4

4. (15pt) Compute the currents  $\dot{I}$ ,  $\dot{I}_1$ ,  $\dot{I}_2$  and  $\dot{V}_C$  in Figure 4.  $R_1=R_2=10\Omega$ ,

$L=31.8\text{mH}$ ,  $C=318\mu\text{F}$ ,  $f=50\text{Hz}$ ,  $\dot{V} = 10\text{V}$ .

5. (10 pt) The circuit and input waveform of  $v_i = 10\sin\omega t$  (V) are shown in Figure 5, sketch the output waveform using the ideal model for the diode.

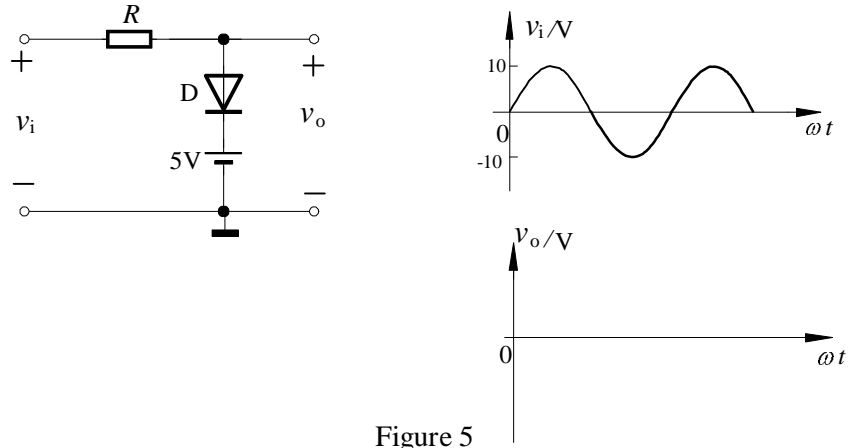


Figure 5

6. (15pt) Find Q-point and gain  $A_v$ , input resistance  $R_i$ , output resistance  $R_o$  for the circuit shown in Figure 6. Assume that the DC current through  $R_2$  is large compared with the expected base current.

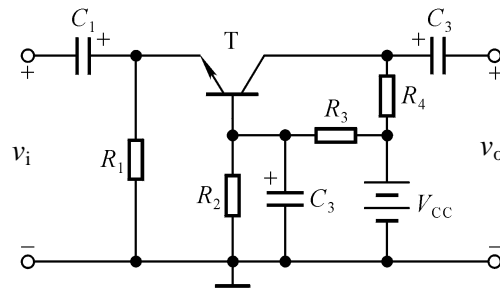


Figure 6

7. (15 pt) Determine the output voltage for the circuit of figure 7

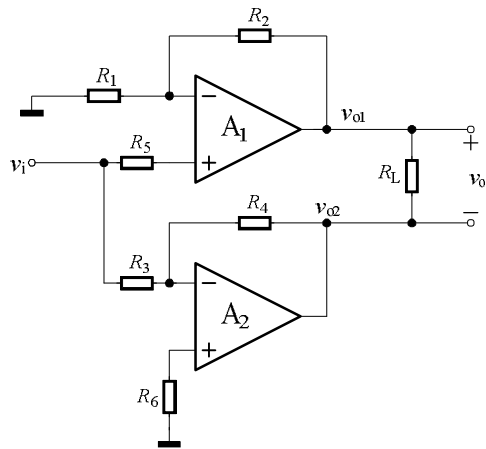


Figure 7

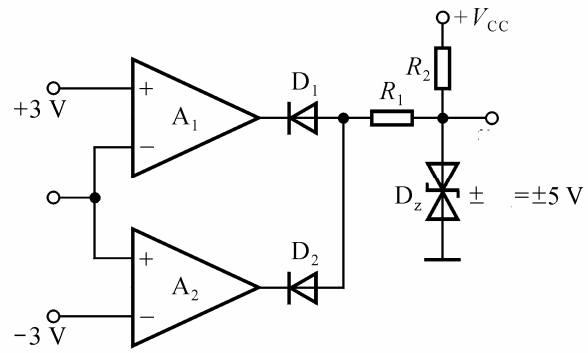


Figure 8

8. (10 pt) The circuit is shown in Figure 8. Find threshold voltages and sketch the transfer characteristics.