

# 《SE-111 电路与模拟电子技术》期末考试试卷(A)

(考试形式： 闭卷 考试时间：2 小时)



《中山大学授予学士学位工作细则》第六条

考试作弊不授予学士学位

方向：\_\_\_\_\_ 姓名：\_\_\_\_\_ 学号：\_\_\_\_\_

注意：答案一定要写在答卷中，写在本试题卷中不给分。本试卷要和答卷一起交回。

1.(10 pt) For the circuit of Figure 1, compute voltage  $V_1$ ,  $V_2$ , and current  $I$

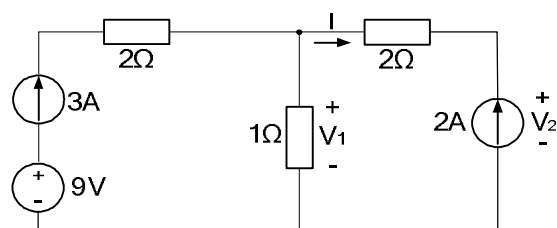


Figure 1

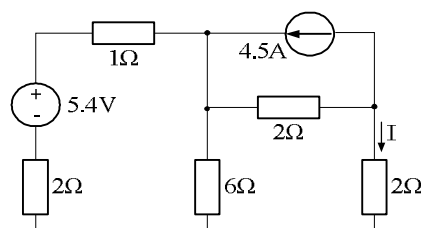


Figure 2

2.(15 pt) Use the superposition theorem to find  $I$  in the circuit shown in Figure 2.

3.(15pt) Find the Thevenin equivalent of the network in Figure 3 viewed from points a、 b.

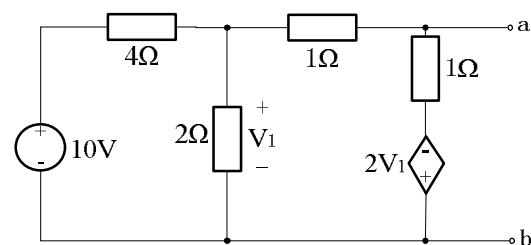


Figure 3

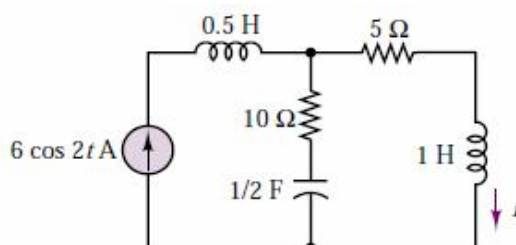


Figure 4

4.(10pt) Compute  $i$  in Figure 4. ( $\arctg 0.1 = 5.7^\circ$ ,  $\arctg 0.067 = 3.8^\circ$ )

5. (10pt) Assume diode's  $V_{on}=0.6(V)$ , sketch the output waveform in Figure 5.

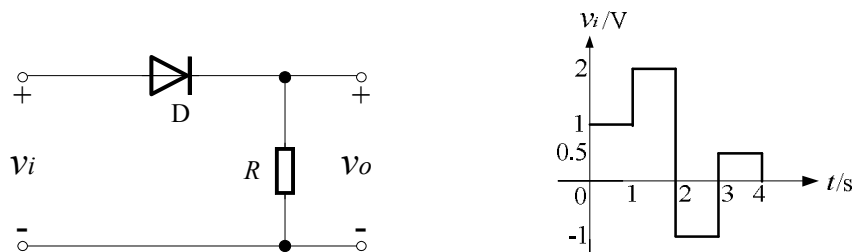


Figure 5

6. (15pt) For the C-E amplifier in Figure 6,

1) Determine the Quiescent Operation Point;

2) Draw the Small-Signal equivalent circuit, Determine the voltage gain and input resistance, output resistance.

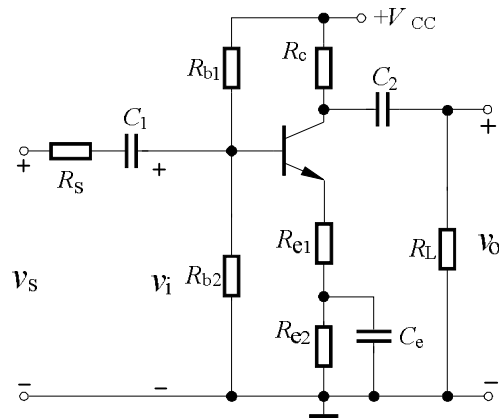


Figure 6

7. (15pt) Determine the output voltage  $v_o$  for the circuit of Figure 7

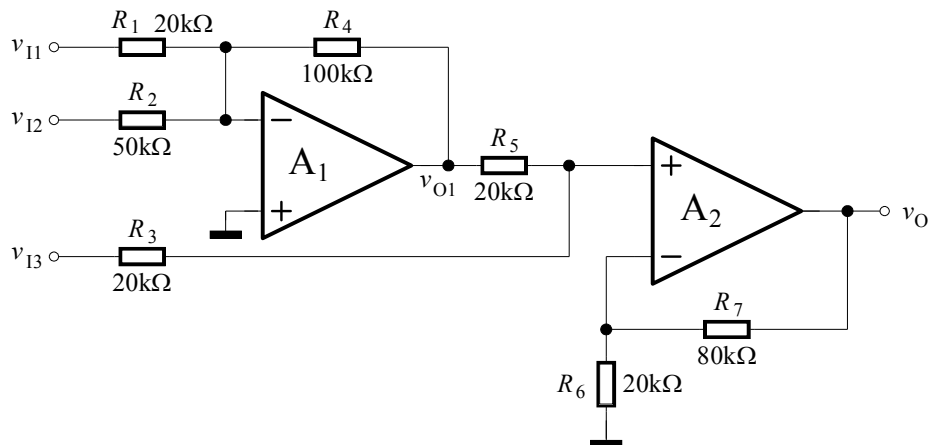


Figure 7

8. (10pt) Design a circuit to  $A_f = \frac{v_o}{v_i} = 0.9$  (Require the input resistance of every signal  $R_i \geq 20k\Omega$ )